

Lab Work 3 (Part 1)

Implementing Sequential Logic

Sequential logic circuits mainly provides storage for a digital system. Thus, for example, it allows implementation of processes that need the previous state of a digital logic.

Only two basic types of sequential logic circuit:

- Latch : level-triggered temporary storage device with 2 stable states
- Flip-flop : edge-triggered storage device


Note: We will be using the button (@reset) switch (instead of the normal toggle DIP-switch). Try to find out why this is a better option.

Implementing Latches

For a basic latch, it needs to have the means to achieve any stable state (HI or LO) at its output and to maintain that output state.

S-R Latch

A basic S-R Latch:

 

Truth table:

S	R	Q_n	$\overline{Q}_n$
0	0	Q_{n-1}	$\overline{Q}_{n-1}$
0	1	0	1
1	0	1	0
1	1	0*	0*


Note: '*' indicates invalid condition

Disclaimer: The image above is extracted from resources available for Digital Fundamentals 11th Edition (Global Edition)

Notice that the invalid condition will happen when the S & R inputs are both at logic 1. In a real digital system, we need to prevent this from happening.

Gated S-R Latch

A gated S-R Latch:

 

Disclaimer: The image above is extracted from resources available for Digital Fundamentals 11th Edition (Global Edition)


Truth table for a S-R Latch:

S	R	EN	Q_n	$\overline{Q}_n$
0	0	0	Q_{n-1}	Q_{n-1}
0	1	0	Q_{n-1}	Q_{n-1}
1	0	0	Q_{n-1}	Q_{n-1}
1	1	0	Q_{n-1}	Q_{n-1}
0	0	1	Q_{n-1}	Q_{n-1}
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1

Note: Output in **BOLD** is an invalid condition.

Gated D Latch

A gated D Latch:

 

Disclaimer: The image above is extracted from resources available for Digital Fundamentals 11th Edition (Global Edition)

Truth table for a gated D Latch:


EN	D	Q_n	$\overline{Q_n}$
0	X	Q_{n-1}	$\overline{Q_{n-1}}$
1	0	0	1
1	1	1	0

Implementing Flip-flops

Unlike latches, flip-flops requires *reference* clock signal that is used to transfer whatever signal at its input to its internal storage (latch).

D Flip-flop

 A D flip-flop (DFF) can be built using two opposite level-triggered gated D latches. This is known as a master slave DFF, as shown in figure below. Is this a positive or negative edge-triggered DFF?



Disclaimer: The image above is obtained from [Wikipedia](https://en.wikipedia.org/wiki/D_flip-flop)

Truth table for a positive edge-triggered DFF:

CLK	D	Q_n	$\overline{Q_n}$
0→1	0	0	1
0→1	1	1	0

The table for negative edge-triggered DFF only differs at CLK column with 1→0 instead of 0→1.

J-K Flip-flop

Truth table for a J-K Flip-flop:

J	K	CLK	Q_n	$\overline{Q_n}$
0	0	0→1	Q_{n-1}	$\overline{Q_{n-1}}$
0	1	0→1	0	1
1	0	0→1	1	0
1	1	0→1	$\overline{Q_{n-1}}$	Q_{n-1}

Notice that, unlike DFF, J-K FF has a toggle mode.

T Flip-flop

The DFF can easily be modified to act as a Flip-flop that toggles on clock edges - by simply connecting the $\bar{Q}$ output to the D input.

Things To Do

THING1 Build an S-R Latch (use NOR gates) and verify.

THING2 Build a gated S-R Latch (use NAND gates) and verify.

THING3 Build a gated D Latch and verify.

THING4 Build a D Flip-flop (DFF) and verify.

THING5 Build a J-K Flip-flop and verify.

THING6 (optional) Try to verify the use of DFF as a frequency divider.

From:

<https://azman.my1matrix.cc/> - Azman @MY1

Permanent link:

<https://azman.my1matrix.cc/doku.php?id=archive:pgt104lab02a>

Last update: **2026/02/08 03:46**

